

Arfan 21d11 Khofiki

23 20500019.

P3 ELM A.

1. Diketahui

$$\left. \begin{aligned} V_s &= 380V \\ f &= 50 \text{ Hz} \end{aligned} \right\} \text{ dari secondary.}$$

$$R_{\text{load}} = 20 \Omega$$

a. Output Voltage Ripple.

$$V_s(\text{CL-N}) = \frac{800}{\sqrt{3}}$$

$$= 219.393V$$

$$V_{m(\text{CL-N})} = 219.393 \times \sqrt{2}$$

$$= 310.268V$$

$$V_{o(\text{dc})} = \frac{(3\sqrt{3} \times V_m)}{2\pi}$$

$$= \frac{(3\sqrt{3} \times 310.268)}{2 \cdot 3.14}$$

$$= 256.719$$

$$V_{o(\text{rms})} = 0.841 \times V_m$$

$$= 0.841 \times 310.268$$

$$= 260.935$$

$$V_{o(\text{ac})} = \sqrt{V_{o(\text{rms})}^2 - V_{o(\text{dc})}^2}$$

$$= \sqrt{260.935^2 - 256.719^2}$$

$$= 46.716V$$

$$\Delta V_o = \frac{V_{o(\text{ac})}}{2\sqrt{2}}$$

$$= \frac{46.716}{2\sqrt{2}}$$

$$= 33.033$$

b. $V_{s(\text{CLM})} = 219.393V$

$$V_{m(\text{CLM})} = 310.268V$$

$$V_{s(\text{c})} = 256.719$$

$$V_{\text{rms}} = 260.936$$

$$FF = \frac{V_{o(\text{rms})}}{V_{s(\text{c})}}$$

$$= \frac{260.936}{256.719}$$

$$= 1.016V$$

c. $R_f = FF^2 (-1)$

$$= 1.016^2 (-1)$$

$$= \sqrt{0.018}$$

$$= 0.129$$

d. $\eta = \frac{P_{o(\text{dc})}}{P_{o(\text{ac})}}$

$$= \frac{(V_{o(\text{dc})} \times I_{o(\text{dc})})}{(V_{o(\text{ac})} \times I_{o(\text{ac})})}$$

$$= \frac{(319.91 \times 15.72)}{(319.58 \times 15.94)} \times 100\%$$

$$= 0.9692\%$$

$$E. V_{(LN)} = 219,315V$$

$$P = 3 \times \frac{V_{(LN)}^2}{R}$$

$$= 3 \times \frac{220^2}{20}$$

$$= \underline{7,129 \text{ kW.}}$$

F. Karena tidak adanya induktansi dan kapasitansi maka besar reaktif powernya = 0.

$$G. Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{R^2} = 20 \Omega$$

$$S = 3 \times \frac{V_{(LN)}^2}{Z}$$

$$= 3 \times \frac{219^2}{20}$$

$$= \underline{7,12 \text{ kW}}$$

$$H. P_f = \frac{P_o \cos(\phi)}$$

$$= \frac{7,129 \text{ kW}}{1}$$

$$= \frac{7,12 \text{ kW}}{1}$$

$$= \underline{1,005 \text{ kW.}}$$