

Arfan Zidul Khoriki

2320500019

2 D3 ELINA.

1) a. $V_o(\text{dc}) = \frac{2V_m}{\pi}$

Siklus positif.

$$\frac{1}{2\pi} \left(\int_0^{\pi} V_m \sin \omega t \, d(\omega t) + \int_{\pi}^{2\pi} -V_m \sin \omega t \, d(\omega t) \right)$$

$$\begin{aligned} V_o(\text{dc}) &= \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t) \\ &= \frac{V_m}{2\pi} \int_0^{\pi} \sin \omega t \, d(\omega t) \\ &= \frac{V_m}{2\pi} \left[-\frac{\cos(\omega t)}{\omega} \right]_0^{\pi}, \quad (T = 2\pi) \\ &= \frac{2V_m}{T} \left[-\frac{\cos(\omega t)}{\omega} \right]_{T/2}^{T/2} \\ &= \frac{2V_m}{\omega T} \left[-\cos(\omega t) \right]_{T/2}^{T/2} \\ &= \frac{2V_m}{\omega T} \left[-\cos \left[\frac{\omega T}{T} \times \frac{T}{2} \right] + \cos(0) \right] \\ &= \frac{2V_m}{\frac{2\pi}{T} \times T} \left[-\cos(\pi) + \cos(0) \right] \\ &= \frac{V_m}{\pi} \left[-\cos(\pi) + \cos(0) \right] \end{aligned}$$

$$V_{o(\text{dc})} = \frac{2V_m}{\pi}$$

Siklus negatif.

$$\begin{aligned} V_o(\text{dc}) &= \frac{1}{2\pi} \int_{\pi}^{2\pi} -V_m \sin \omega t \, d(\omega t), \quad (T_1 < \omega t \leq 2\pi) \\ &= \frac{V_m}{2\pi} \int_{\pi}^{2\pi} -\sin \omega t \, d(\omega t) \\ &= \frac{2V_m}{2\pi} \left[-\frac{(-\cos \omega t)}{\omega} \right]_{\pi}^{2\pi}, \quad (T = 2\pi) \\ &= \frac{2V_m}{T} \left[\cos \omega t \right]_{T/2}^T, \quad (\omega = \frac{2\pi}{T}) \end{aligned}$$

$$V_o(dc) = \frac{2V_m}{\pi} \left[\cos\left(\frac{2\pi}{T} \times \frac{T}{2}\right) + \left[\cos\left(\frac{2\pi}{T} \times T\right) \right] \right]$$

$$\begin{aligned} V_o(dc) &= \frac{2V_m}{\pi} [\cos\pi + \cos 2\pi] \\ &= \frac{2V_m}{\pi} [1 + (-1)] \\ &= 0. \end{aligned}$$

1) B. $V_o(rms) = V_s(rms)$.

$$V_o(rms) = \sqrt{\frac{1}{2\pi} \left(\int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t) + \int_{\pi}^{2\pi} (-V_m \sin \omega t)^2 d(\omega t) \right)}$$

atau

$$V_o(rms) = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t)}$$

Menghitung Rms karena nilai dari Rms akan selalu sama untuk setiap periode $0 < \omega t < \pi$ sampai $\pi < \omega t \leq 2\pi$

$$\begin{aligned} V_o(rms) &= \sqrt{\frac{1}{2\pi} \int_0^{\pi} V^2 dt} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t)} \\ &= \frac{1}{\frac{T}{2}} \int_0^{T/2} (V_m \sin \omega t)^2 d(\omega t) \quad (T = 2\pi) \\ &= \frac{2}{T} \int_0^{T/2} V_m^2 \sin^2 \omega t d(\omega t) \\ &= \frac{2V_m}{T} \int_0^{T/2} \left[\frac{-\cos(2\omega t)}{2} \right] d(\omega t) \\ &= \frac{V_m}{T} \left[\omega t - \frac{\sin(2\omega t)}{2\omega} \right]_0^{T/2} \\ &= \frac{V_m}{T} \left[\frac{T}{2} - \frac{\sin\left(2 \cdot \frac{2\pi}{T} \times \frac{T}{2}\right)}{2\omega} - 0 + \frac{\sin(0)}{2\omega} \right] \\ &= \frac{V_m}{T} \times \frac{T}{2} \\ &= \frac{V_m}{\sqrt{2}} \quad (V_s(rms) = \frac{V_m}{\sqrt{2}}) \end{aligned}$$

$$\underline{V_o(rms) = V_s(rms)}$$

3. Diketahui :

$$V_{oc(rms)} = 220V$$

$$\text{frequency} = 50 \text{ Hz}$$

$$\text{Trafo stepdown} = 6:1$$

a) Diket :

$$R = 100 \text{ ohm}$$

$$f_f = ?$$

$$P_f = ?$$

$$AV_0 = ?$$

$$I_0(d.c) = \frac{V_0(d.c)}{R}$$

$$= \frac{32,8}{100} = 0,328 \text{ A}$$

$$P_0(d.c) = V_0(d.c) \times I_0(d.c)$$

$$= 32,8 \times 0,328$$

$$= 10,75 \text{ WATT}$$

$$P_f = \frac{V_0(rms)}{V_s(rms)} = \frac{36,6}{30,6} = 1$$

$$I_0(rms) = \frac{I_0(d.c)}{(\sqrt{2} \times 0,636)} = \frac{0,328}{0,899} = 0,364 \text{ A}$$

$$P_0(rms) = V_0(rms) \times I_0(rms)$$

$$= 36,6 \times 0,364 = 13,3 \text{ watt}$$

$$\text{Efisiensi} = \frac{P_0(d.c)}{P_0(rms)} = \frac{10,75}{13,3}$$

$$= 0,8 = 80 \%$$

Metoda.

$$\frac{N_p}{N_s} = \frac{V_p}{V_s}$$

$$\frac{6}{1} = \frac{220}{V_s}$$

$$V_s = 36,6 \text{ V}$$

$$V_s(rms)_{max} = 36,6 \times \sqrt{2} = 51,7$$

$$V_0(d.c) = 0,636 \times V_s$$

$$= 0,636 \times 51,7$$

$$= 32,8 \text{ V}$$

$$V_0(rms) = V_s(rms)$$

$$V_0(rms) = 36,6 \text{ V}$$

$$V_{oc} = \sqrt{(V_0(rms))^2 - (V_0(d.c))^2}$$

$$= \sqrt{(36,6)^2 - (32,8)^2}$$

$$= 10,2 \text{ V}$$

Metoda

$$f_f = \frac{V_0(rms)}{V_0(d.c)} = \frac{36,6}{32,8} = 1,1$$

$$P_f = \frac{V_{oc}}{V_{oc}} = \frac{10,2}{32,8} = 0,31$$

$$AV_0 = 2\sqrt{2} \times V_{oc}$$

$$= 2\sqrt{2} \times 10,2$$

$$= 45,8 \text{ V}$$

3) B. Dipegang kapasitor filter sebesar 1000 μ F

Maka

$$\begin{aligned}\Delta V_o &= \frac{V_{\max}}{2 \cdot f \cdot R \cdot C} \\ &= \frac{V_{\text{rms}} \times \sqrt{2}}{2 \cdot 10 \cdot 100 \cdot 10^{-3}} \\ &= 5,176 \text{ V}\end{aligned}$$

$$\begin{aligned}V_o(f) &= V_m - \left[\frac{\Delta V_o}{2} \right] \\ &= 85,6 \times \sqrt{2} - \frac{5,176}{2} \\ &= 99,1 \text{ V}\end{aligned}$$

$$V_{ac} : \left[\frac{\Delta V_o}{2\sqrt{2}} \right] = \left[\frac{5,176}{2} \right] = 2,58 \text{ V}$$

$$f_f = \frac{V_{\text{rms}}}{V_{dc}} =$$

$$\begin{aligned}V_{\text{rms}} &= \sqrt{V_{ac}^2 + V_{dc}^2} \\ &= \sqrt{(2,58)^2 + (99,1)^2} \\ &= 99,1 \text{ V}\end{aligned}$$

$$f_f = \frac{V_{\text{rms}}}{V_{dc}} = \frac{99,1}{99,1} = 1$$

$$R_f = \frac{V_{ac}}{V_{dc}} = \frac{2,58}{99,1} = 0,02$$

3) C. jika $\Delta V_o = 0,5\%$

$$\begin{aligned}\Delta V_o &= 0,5\% \times V_{\text{rms}} \\ &= 0,5\% \times 51,7 \\ &= 0,25 \text{ V}\end{aligned}$$

$$\Delta V_o = \frac{V_{\max}}{2 \cdot f \cdot R \cdot C}$$

$$0,25 = \frac{51,7}{100 \cdot 100 \cdot C}$$

$$0,25 \times (100 \cdot C) = 51,7$$

$$2500 C = 51,7$$

$$C = 0,02 \text{ F}$$

$$\begin{aligned}V_{dc} &= V_m - \frac{\Delta V_o}{2} \\ &= 85,7 - \frac{0,25}{2} \\ &= 51,57 \text{ V}\end{aligned}$$

$$\begin{aligned}V_{ac} &= \Delta V_o \times (2\sqrt{2})^{-1} \\ &= 0,25 \times (2\sqrt{2})^{-1} = 0,088 \text{ V}\end{aligned}$$

$$\begin{aligned}V_{\text{rms}} &= \sqrt{V_{ac}^2 + V_{dc}^2} \\ &= 51,57 \text{ V}\end{aligned}$$

$$f_f = 1$$

$$R_f = 0,001$$

3) D. jika ripple faktor \leq standart Internasional. maka.

$$RF = \leq 1\%$$

Sehingga.

$$RF = 1\% \times 32.8 \\ = 0.328\%$$

$$RF = \frac{V_{ac}}{V_{dc}}$$

$$0.328 = \frac{V_{ac}}{32.8}$$

$$V_{ac} = 10.75 \text{ V.}$$

$$\Delta V_o = 2\sqrt{2} \times 10.75 \\ = 30.4 \text{ V.}$$

$$\Delta V_o = \frac{V_m}{2fRC}$$

$$30.4 = \frac{51.7}{2 \times 100. \text{ C.}}$$

$$30.4 \cdot 2 \cdot (5.100) \text{ C} = 51.7$$

$$304000 \text{ C} = 51.7$$

$$\text{C} = 0.17 \text{ mF.}$$

$$V_{dc} = V_m - \frac{\Delta V_o}{2}$$

$$= 51.7 - \frac{30.4}{2} \\ = 36.5 \text{ V.}$$

$$V_{rms} = \sqrt{V_{dc}^2 + V_{ac}^2}$$

$$= \sqrt{10.75^2 + 36.5^2} \\ = 38.2 \text{ V.}$$

$$F_f = 0.8$$

$$RF = 0.8$$

* jika $RF = 0.005 V_{max}$.

$$RF = 0.005 \times V_m \\ = 0.005 \times 51.7 \\ = 0.258$$

$$RF = \frac{V_{ac}}{V_{dc}}$$

$$0.25 = \frac{V_{ac}}{32.8}$$

$$V_{ac} = 8.2 \text{ V.}$$

$$\Delta V_o = 2\sqrt{2} \times 8.2 \\ = 23.1 \text{ V}$$

$$\Delta V_o = \frac{V_m}{2fRC}$$

$$23.1 = \frac{51.7}{2 \times 100 \text{ C.}}$$

$$\text{C} = 0.22 \text{ mF}$$

$$V_{dc} = V_m - \frac{\Delta V_o}{2}$$

$$= 51.7 - \frac{23.1}{2}$$

$$= 40.1$$

$$V_{rms} = \sqrt{V_{ac}^2 + V_{dc}^2}$$

$$= \sqrt{(8.2)^2 + 40.1^2} \\ = 40.9 \text{ V.}$$

$$F_f = 0.1$$

$$RF = \frac{V_{rms}}{V_{dc}}$$

$$= \frac{40.9}{40.1}$$

$$= 1.019$$

3) E). Dari praktikum yang telah dilaksanakan.

$$V_{dc} = 33 \text{ V}$$

$$V_{dc(rms)} = 36,67 \text{ V}$$

$$V_{sumber} = 311,12 \text{ V}$$

$$I_{dc(rms)} = 0,366$$

$$I_{dc} = 0,33$$

Maka:

$$\begin{aligned} V_{ac} &= \sqrt{(V_{o(dc)})^2 + (V_{o(rms)})^2} \\ &= \sqrt{36,67^2 + 33^2} \\ &= 49,9 \end{aligned}$$

$$\begin{aligned} FF &= \frac{V_{rms}}{V_{dc}} \\ &= \frac{36,67}{33} = 1,1 \end{aligned}$$

$$\begin{aligned} RF &= \frac{V_{ac}}{V_{dc}} \\ &= \frac{49,9}{33} = 1,51 \end{aligned}$$

$$\begin{aligned} \Delta V_o &= 2\sqrt{2} \times V_{dc} \\ &= 99,9 \text{ V} \end{aligned}$$

$$\begin{aligned} P_{dc} &= V_{dc} \times I_{dc} \\ &= 33 \times 0,33 \\ &= 10,89 \text{ Watt} \end{aligned}$$

$$\begin{aligned} P_o &= V_o \times I_o \\ &= 36,67 \times 0,366 \\ &= 13,421 \text{ Watt} \end{aligned}$$

$$\begin{aligned} \eta &= \frac{P_{o(dc)}}{P_{o(ac)}} \times 100\% \\ &= 81\% \end{aligned}$$

* Untuk $R = 100 \text{ Ohm}$.

$$V_{dc} = 47,9 \text{ V}$$

$$V_{rms} = 48,15 \text{ V}$$

$$I = 1,71$$

$$V_s = 51,86 \text{ V}$$

$$\begin{aligned} \Delta V_o &= \frac{V_s}{2fRC} \\ &= \frac{56,95}{2fRC} \\ &= 5,695 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{dc} &= V_m - \frac{\Delta V_o}{2} \\ &= 56,95 - \frac{5,695}{2} \\ &= 59,1 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{ac} &= \frac{\Delta V_o}{2\sqrt{2}} \\ &= \frac{5,695}{2\sqrt{2}} = 2,01 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{rms} &= \sqrt{(59,1)^2 + (2,01)^2} \\ &= 59,1 \text{ V} \end{aligned}$$

$$FF = 1,01$$

$$RF = 0,642$$

3). E. Dengan kapasitor filter. dan R.

Diketahui

$$V_{c(max)} = 56,97V.$$

$$V_{dc} = 50,01V$$

$$V_{rms} = V_{orms} = 50,07V.$$

~~V_{max}~~ :

$$\begin{aligned} \Delta V_o &= \frac{V_{c(max)}}{2fRC} \\ &= \frac{51,96}{2 \cdot 50 \cdot 100 \cdot 0,02} \\ &= 0,289. \end{aligned}$$

$$\begin{aligned} V_{ac} &= \frac{\Delta V_o}{2\sqrt{2}} = \frac{0,289}{2\sqrt{2}} \\ &= 0,100. \end{aligned}$$

$$\begin{aligned} FF &= \frac{V_{orms}}{V_{dc}} \\ &= \frac{50,07}{50,01} \\ &= 1,001 \end{aligned}$$

$$RF = \frac{V_{ac}}{V_{dc}} = 0,0020.$$

Data dari percobaan.

$$V_{dc} = 42,55V.$$

$$V_{orms} = 43,36V.$$

$$\begin{aligned} \Delta V_o &= \frac{V_{c(max)}}{2fRC} \\ &= \frac{51,96}{2 \cdot 50 \cdot 100 \cdot 0,168 \times 10^{-3}} \end{aligned}$$

$$\Delta V_o = 30,93V.$$

$$\begin{aligned} V_{ac} &= \frac{\Delta V_o}{2\sqrt{2}} \\ &= \frac{30,93}{2\sqrt{2}} \\ &= 10,968V. \end{aligned}$$

$$FF = \frac{V_{rms}}{V_{dc}} = \frac{43,6}{42,5} = 1,019$$

$$RF = \frac{V_{ac}}{V_{dc}} = \frac{10,968}{42,55} = 0,259.$$